


CS 61C: Great Ideas in Computer Architecture

Lecture 12: *Single-Cycle CPU, Datapath & Control Part 2*

Instructor: Sagar Karandikar
sagark@eecs.berkeley.edu

<http://inst.eecs.berkeley.edu/~cs61c>

Midterm 1 Results

 

- You may submit regrade requests by Wednesday @ 23:59:59
- Solutions posted on Piazza

If you didn't do as well as you'd hoped

- You can still get an A with the clobber
 - 3 days preceding the final: there are no assignments, labs and discussions are OH
- Lots of resources to help:
 - 12 hours of OH/week
 - Go earlier in the week for conceptual questions (or come to mine)
 - Guerrilla section every Thursday (goes over exam-style problems)
 - You may go to multiple discussions (good to hear things from multiple perspectives)

Levels of Representation/ Interpretation

High Level Language
Program (e.g., C)

Compiler

Assembly Language
Program (e.g., MIPS)

Assembler

Machine Language
Program (MIPS)

*Machine
Interpretation*

Hardware Architecture Description
(e.g., block diagrams)

*Architecture
Implementation*


Logic Circuit Description
(Circuit Schematic Diagrams)

```
temp = v[k];  
v[k] = v[k+1];  
v[k+1] = temp;
```


```
lw    $t0, 0($2)  
lw    $t1, 4($2)  
sw    $t1, 0($2)  
sw    $t0, 4($2)
```

Anything can be represented
as a *number*,
i.e., data or instructions
 
```
0000 1001 1100 0110 1010 1111 0101 1000  
1010 1111 0101 1000 0000 1001 1100 0110  
1100 0110 1010 1111 0101 1000 0000 1001  
0101 1000 0000 1001 1100 0110 1010 1111
```



No More Magic!

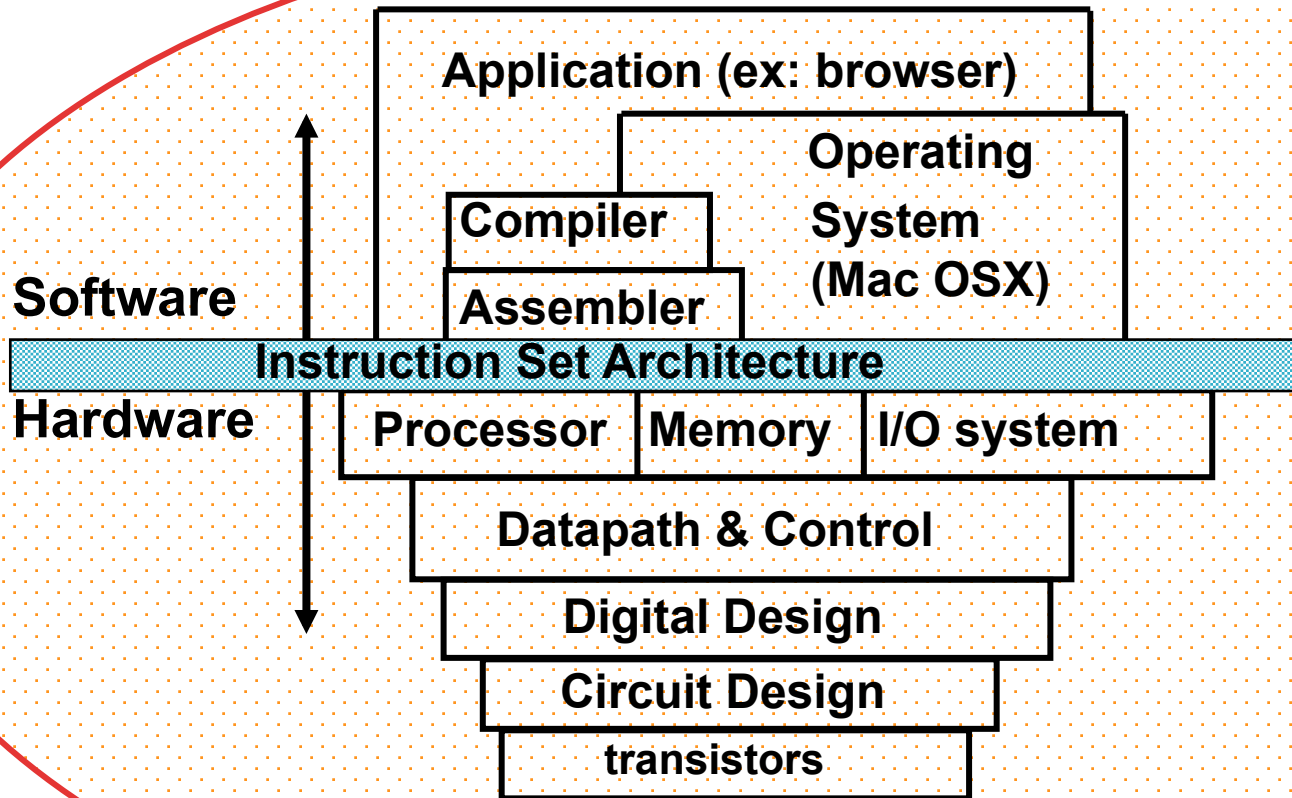

CS61A

CS61B

CS61C ✓

CS61C ✓

CS61C ✓

CS61C ←

CS61C ✓

EE40

Phys 7B

Last time: Processor Design: 3 of 5 steps

Step 1: Analyze instruction set to determine datapath requirements

- Meaning of each instruction is given by register transfers
- Datapath must include storage element for ISA registers
- Datapath must support each register transfer

Step 2: Select set of datapath components & establish clock methodology


Step 3: Assemble datapath components that meet the requirements

Step 4: Analyze implementation of each instruction to determine setting of control points that realizes the register transfer

Step 5: Assemble the control logic

Step 1: The MIPS Instruction Formats

 - All MIPS instructions are 32 bits long. 3 formats:



- The different fields are:
 - **op**: operation (“opcode”) of the instruction
 - **rs, rt, rd**: the source and destination register specifiers
 - **shamt**: shift amount
 - **funct**: selects the variant of the operation in the “op” field
 - **address / immediate**: address offset or immediate value
 - **target address**: target address of jump instruction

Step 1: Register Transfer Level (RTL)

- Colloquially called “Register Transfer Language”
- RTL gives the meaning of the instructions
- All start by fetching the instruction itself

```
{op , rs , rt , rd , shamt , funct} ← MEM[ PC ]
```

```
{op , rs , rt , Imm16} ← MEM[ PC ]
```

Inst Register Transfers

```
ADDU    R[rd] ← R[rs] + R[rt]; PC ← PC + 4
```

```
SUBU    R[rd] ← R[rs] - R[rt]; PC ← PC + 4
```

```
ORI     R[rt] ← R[rs] | zero_ext(Imm16); PC ← PC + 4
```

```
LOAD    R[rt] ← MEM[ R[rs] + sign_ext(Imm16) ]; PC ← PC + 4
```

```
STORE   MEM[ R[rs] + sign_ext(Imm16) ] ← R[rt]; PC ← PC + 4
```




```
BEQ     if ( R[rs] == R[rt] )  
         PC ← PC + 4 + {sign_ext(Imm16), 2'b00}  
      else PC ← PC + 4
```


Step 1: Requirements of the Instruction Set

- Memory (MEM)
 - Instructions & data (will use one for each)
- Registers (R: 32, 32-bit wide registers)
 - Read RS
 - Read RT
 - Write RT or RD
- Program Counter (PC)
- Extender (sign/zero extend)
- Add/Sub/OR/etc unit for operation on register(s) or extended immediate (ALU)
- Add 4 (+ maybe extended immediate) to PC
- Compare registers?

Step 2: Components of the Datapath

   - Combinational Elements
- Storage Elements + Clocking Methodology
- Building Blocks




Step 2: ALU Needs for MIPS-lite + Rest of MIPS

- Addition, subtraction, logical OR, ==:
 `ADDU R[rd] = R[rs] + R[rt]; ...`
 `SUBU R[rd] = R[rs] - R[rt]; ...`
 `ORI R[rt] = R[rs] | zero_ext(Imm16)...`
 `BEQ if (R[rs] == R[rt])...`
- Test to see if output == 0 for any ALU operation gives == test. How?
- P&H also adds AND, Set Less Than (1 if $A < B$, 0 otherwise)
- ALU follows Chapter 5


Step 2: Storage Element: Idealized Memory

- “Magic” Memory
 - One input bus: Data In
 - One output bus: Data Out
- Memory word is found by:
 - For Read: Address selects the word to put on Data Out
 - For Write: Set Write Enable = 1: address selects the memory word to be written via the Data In bus
- Clock input (CLK)
 - CLK input is a factor ONLY during write operation
 - During read operation, behaves as a combinational logic block: Address valid \Rightarrow Data Out valid after “access time”

 


Step 2: Storage Element: Register (Building Block)

 - Similar to D Flip Flop except
 - N-bit input and output
 - Write Enable input
- Write Enable:
 - Negated (or deasserted) (0): Data Out will not change
 - Asserted (1): Data Out will become Data In on positive edge of clock




Step 2: Storage Element: Register File

- Register File consists of 32 registers:
 - Two 32-bit output busses: busA and busB
 - One 32-bit input bus: busW
- Register is selected by:
 - RA (number) selects the register to put on busA (data)
 - RB (number) selects the register to put on busB (data)
 - RW (number) selects the register to be written via busW (data) when Write Enable is 1
- Clock input (clk)
 - Clk input is a factor ONLY during write operation
 - During read operation, behaves as a combinational logic block:
 - RA or RB valid \Rightarrow busA or busB valid after “access time.”

 


Example: RegFile with 8 Registers

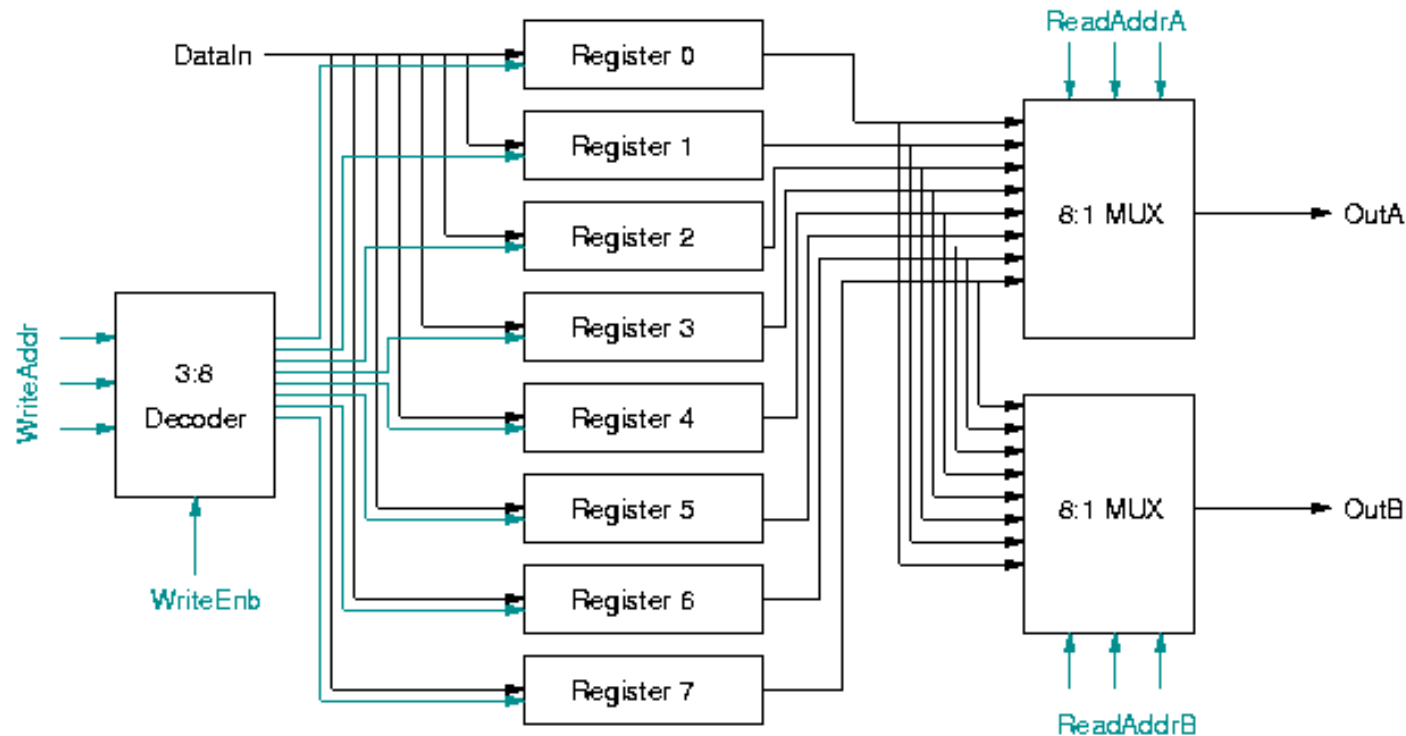

Gray lines are 1-bit signals

Black lines are 10-bit signals


Step 2: Clocking Methodology

 

- Storage elements clocked by same edge
- Flip-flops (FFs) and combinational logic have some delays
 - Gates: delay from input change to output change
 - Signals at FF D input must be stable before active clock edge to allow signal to travel within the FF (set-up time), and we have the usual clock-to-Q delay
- “Critical path” (longest path through logic) determines length of clock period


Step 3a: Instruction Fetch Unit

 - Register Transfer Requirements \Rightarrow Datapath Assembly
- Instruction Fetch
- Read Operands and Execute Operation
- Common RTL operations
 - Fetch the Instruction:
 $\text{mem}[\text{PC}]$
 - Update the program counter:
 - Sequential Code:
 $\text{PC} \leftarrow \text{PC} + 4$
 - Branch and Jump:
 $\text{PC} \leftarrow \text{“something else”}$




Step 3b: Add & Subtract

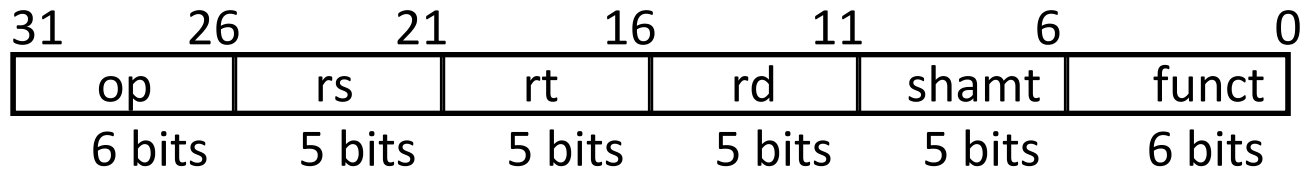- $R[rd] = R[rs] \text{ op } R[rt]$ (`addu rd,rs,rt`)
 - Ra, Rb, and Rw come from instruction's Rs, Rt, and Rd fields




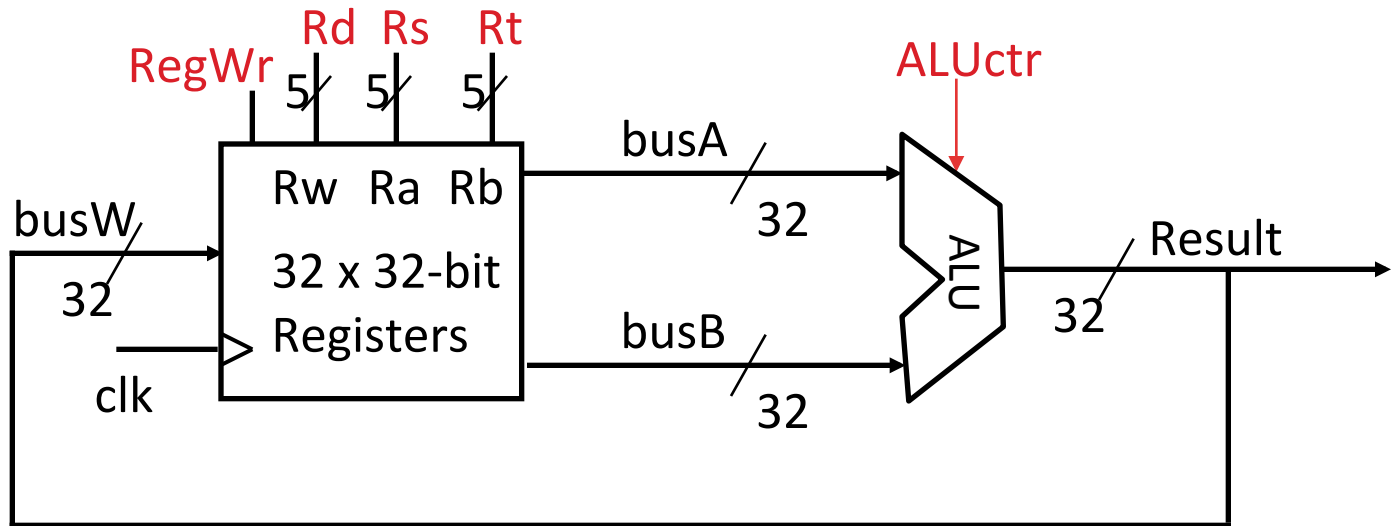- **ALUctr** and **RegWr**: control logic after decoding the instruction



- ... Already defined the register file & ALU

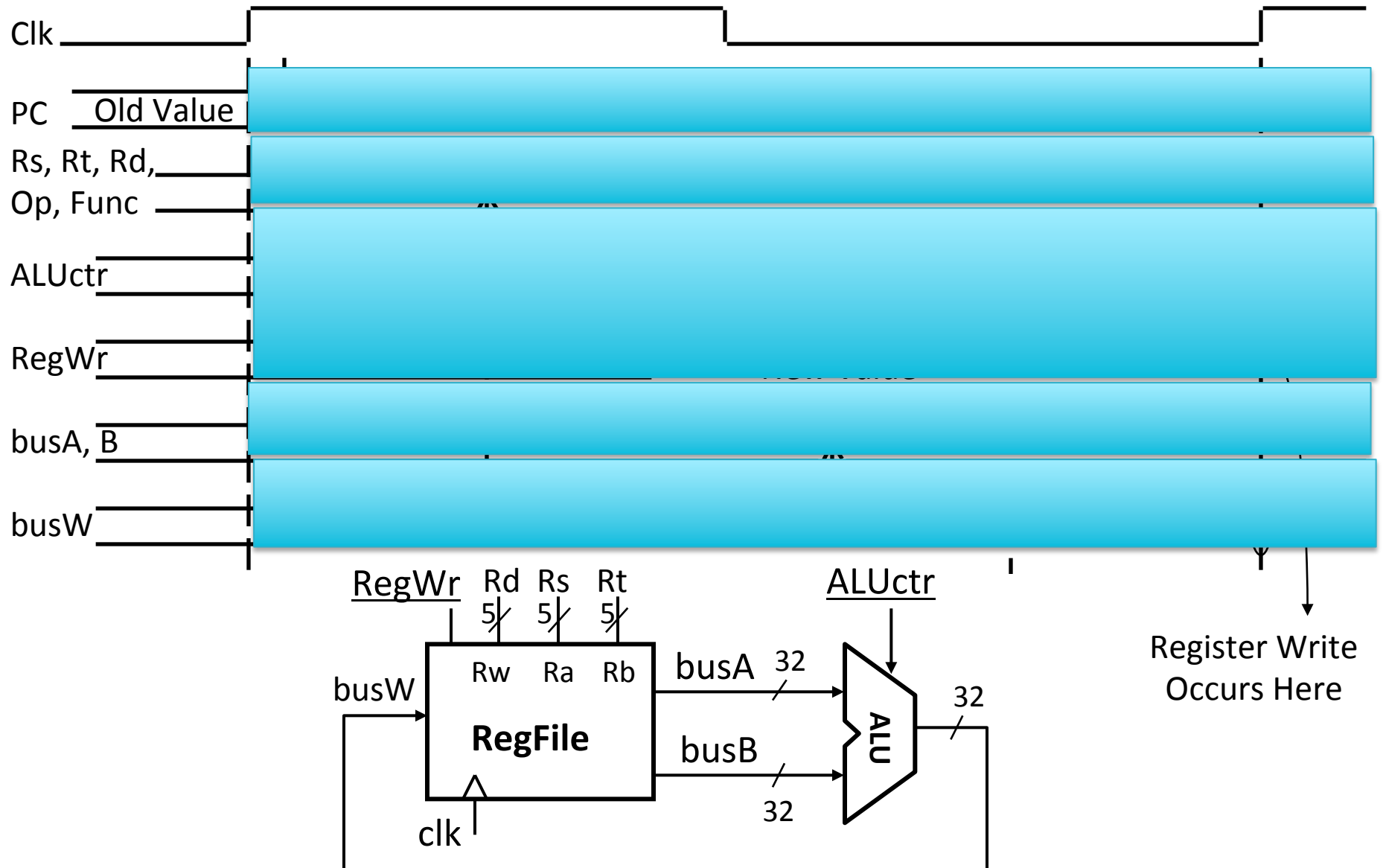Register-Register Timing: One Complete Cycle (Add/Sub)



Peer Instruction

1. We should use the main ALU to compute $PC=PC+4$ in order to save some gates
2. The ALU is inactive for memory reads (loads) or writes (stores).

	1	2
A	F	F
B	F	T
C	T	F
D	T	T

Administrivia

- HW3 Out
 - Covers SDS topics from last week
- Proj 2-2 out
 - Make sure you test your code on hive machines, that's where we'll grade them


Break

End of the review

- Now let's finish steps 3, 4, and 5
- By the end of today, you'll know how an entire computer works!

3c: Logical Op (or) with Immediate

 
- $R[\text{rt}] = R[\text{rs}] \text{ op ZeroExt}[\text{imm16}]$



3d: Load Operations

- $R[\text{rt}] = \text{Mem}[R[\text{rs}] + \text{SignExt}[\text{imm16}]]$


Example: `lw rt,rs,imm16`

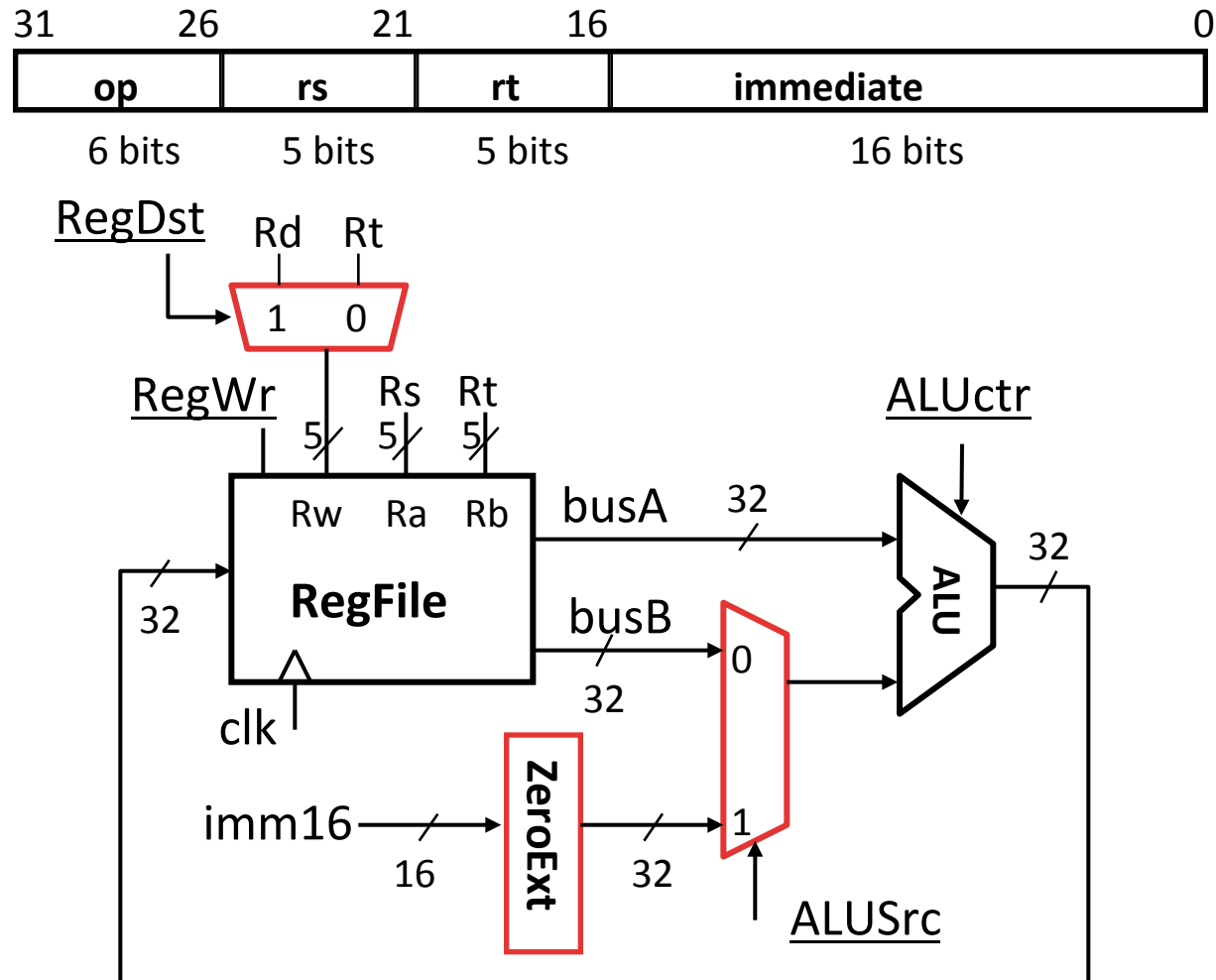

3d: Load Operations

- $R[\text{rt}] = \text{Mem}[R[\text{rs}] + \text{SignExt}[\text{imm16}]]$



Example: `lw rt, rs, imm16`

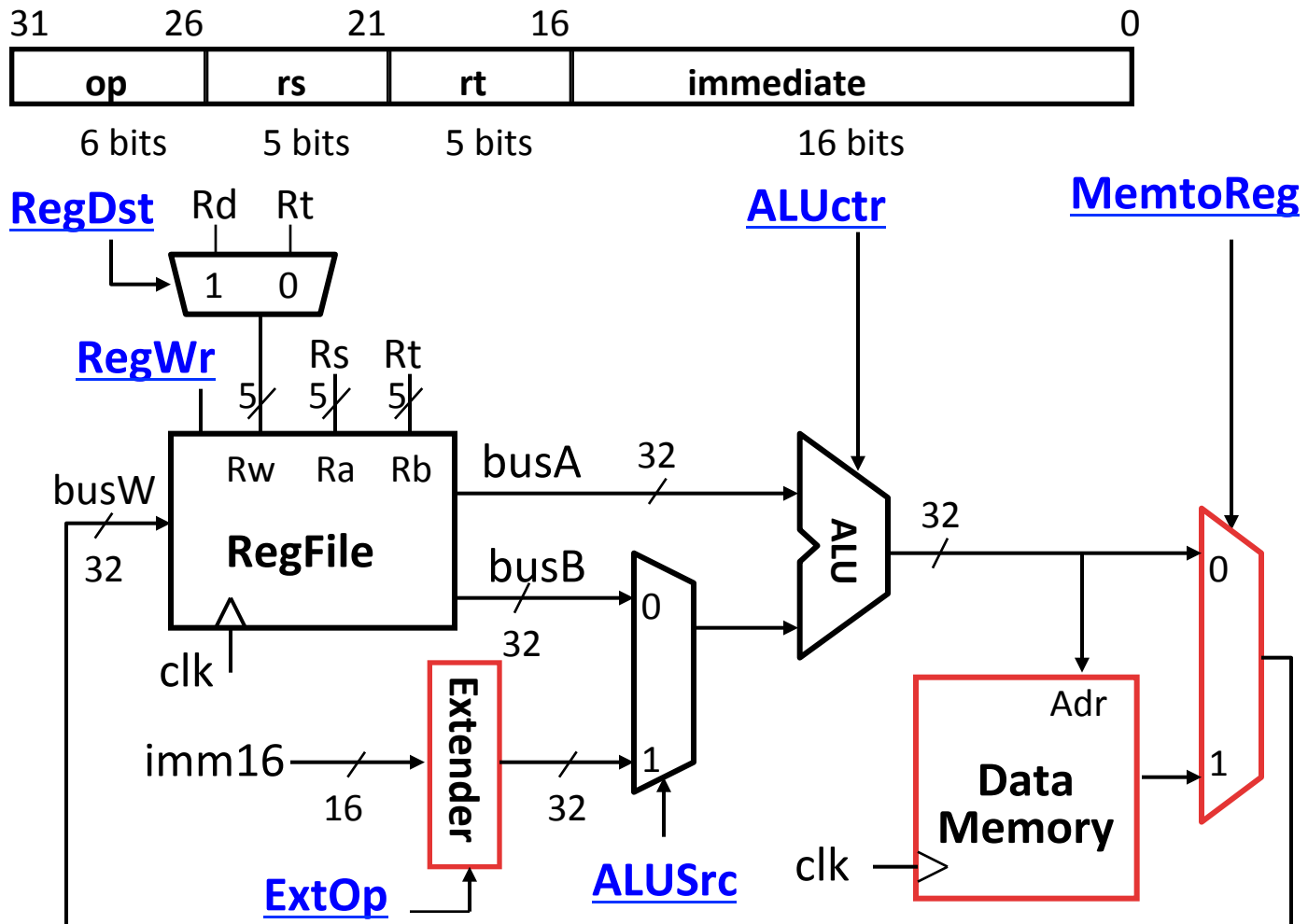

3e: Store Operations

- Mem[R[rs] + SignExt[imm16]] = R[rt]



Ex.: sw rt, rs, imm16

  


3e: Store Operations

- $\text{Mem}[\text{R}[\text{rs}] + \text{SignExt}[\text{imm16}]] = \text{R}[\text{rt}]$

Ex.: `sw rt, rs, imm16`

  

3f: The Branch Instruction

 


`beq rs, rt, imm16`

- `mem[PC]` Fetch the instruction from memory
- `Equal = (R[rs] == R[rt])` Calculate branch condition
- if (`Equal`) Calculate the next instruction's address
 - $PC = PC + 4 + (\text{SignExt}(\text{imm16}) \times 4)$
- else
 - $PC = PC + 4$


Datapath for Branch Operations

beq rs, rt, imm16

 


Datapath generates condition (Equal)

Inst Address

 


Already have mux, adder, need special sign extender for PC, need equal compare (sub?)

Instruction Fetch Unit including Branch

 

 - if (Zero == 1) then $PC = PC + 4 + \text{SignExt}[\text{imm16}] * 4$; else $PC = PC + 4$




- How to encode nPC_sel?
 - Direct MUX select?
 - Branch inst. / not branch inst.
- Let's pick 2nd option

nPC_sel	zero?	MUX
0	x	0
1	0	0
1	1	1

Q: What logic gate?



 Putting it All Together: A Single Cycle Datapath



Processor Design: 5 steps

Step 1: Analyze instruction set to determine datapath requirements

- Meaning of each instruction is given by register transfers
- Datapath must include storage element for ISA registers
- Datapath must support each register transfer

Step 2: Select set of datapath components & establish clock methodology


Step 3: Assemble datapath components that meet the requirements

Step 4: Analyze implementation of each instruction to determine setting of control points that realizes the register transfer


Step 5: Assemble the control logic

Datapath Control Signals

 
- ExtOp: “zero”, “sign”
- ALUsrc: 0 \Rightarrow regB;
1 \Rightarrow imm
- ALUctr: “ADD”, “SUB”, “OR”
- MemWr: 1 \Rightarrow write memory
- MemtoReg: 0 \Rightarrow ALU; 1 \Rightarrow Mem
- RegDst: 0 \Rightarrow “rt”; 1 \Rightarrow “rd”
- RegWr: 1 \Rightarrow write register



Given Datapath: RTL \rightarrow Control

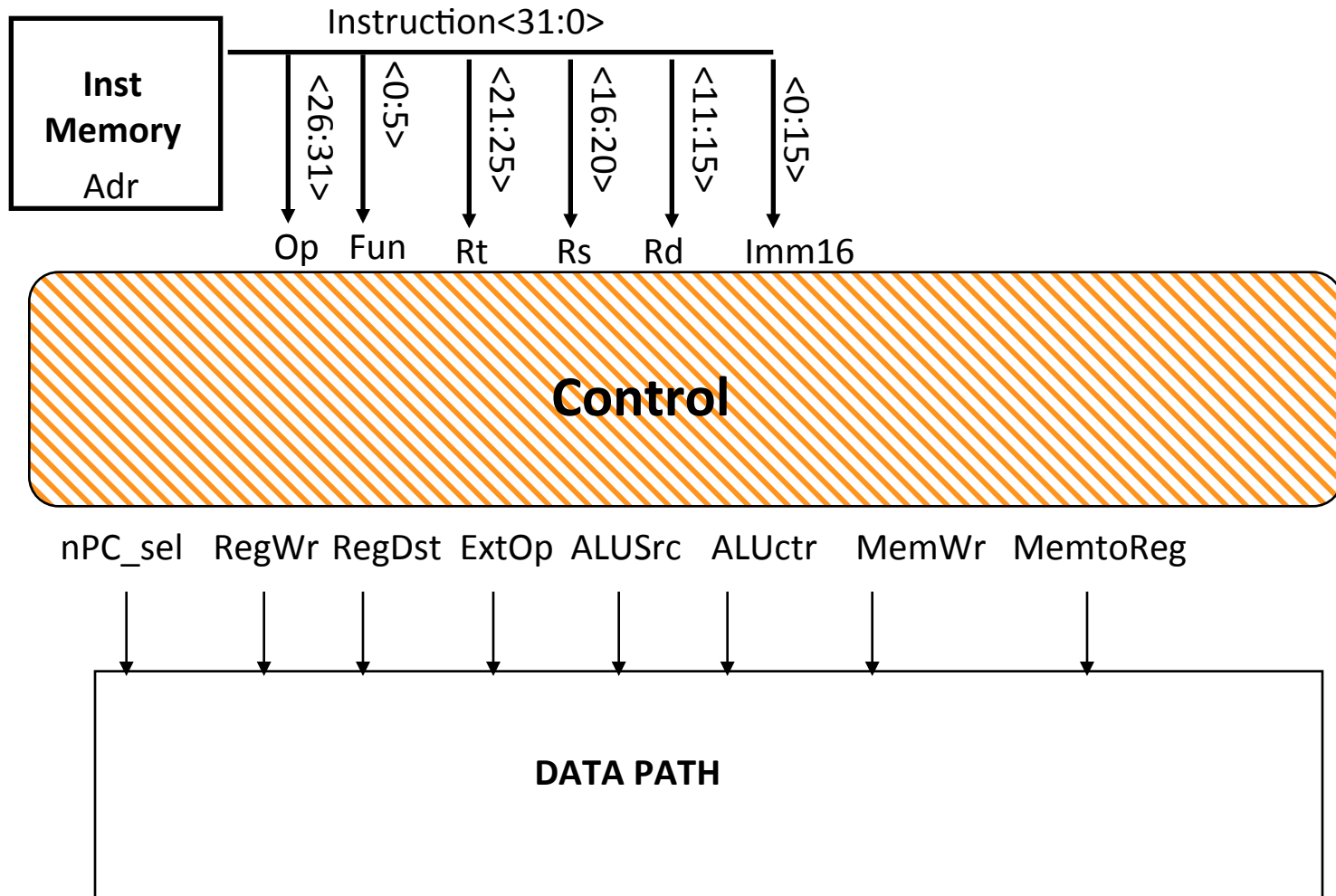

RTL: The Add Instruction

 

add rd, rs, rt


- MEM[PC] Fetch the instruction from memory
- $R[rd] = R[rs] + R[rt]$ The actual operation
- $PC = PC + 4$ Calculate the next instruction's address

Instruction Fetch Unit at the Beginning of Add


- Fetch the instruction from Instruction

memory: $\text{Instruction} = \text{MEM}[\text{PC}]$


- same for all instructions

 

Single Cycle Datapath during Add

 


$$R[rd] = R[rs] + R[rt]$$

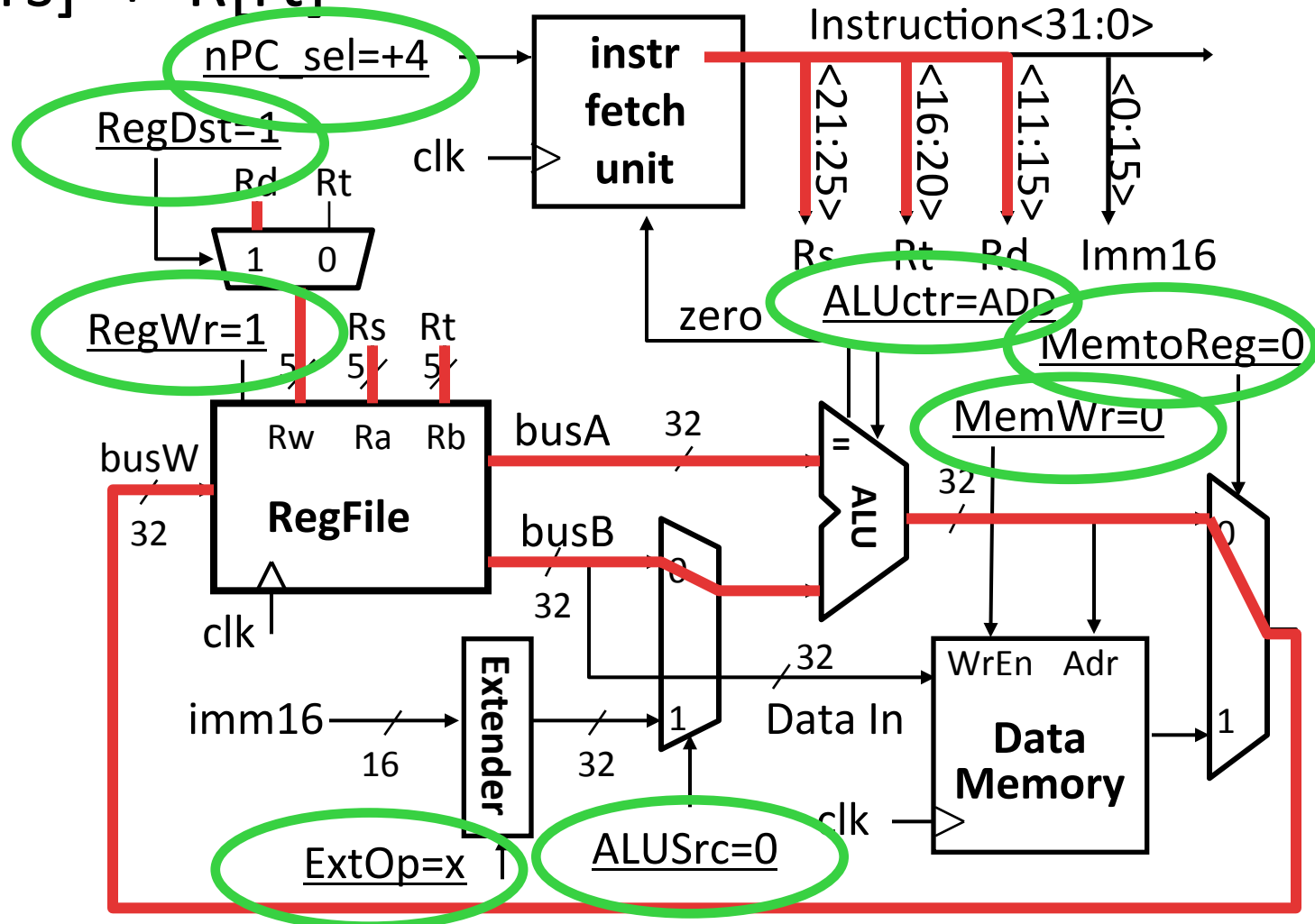

Instruction Fetch Unit at End of Add

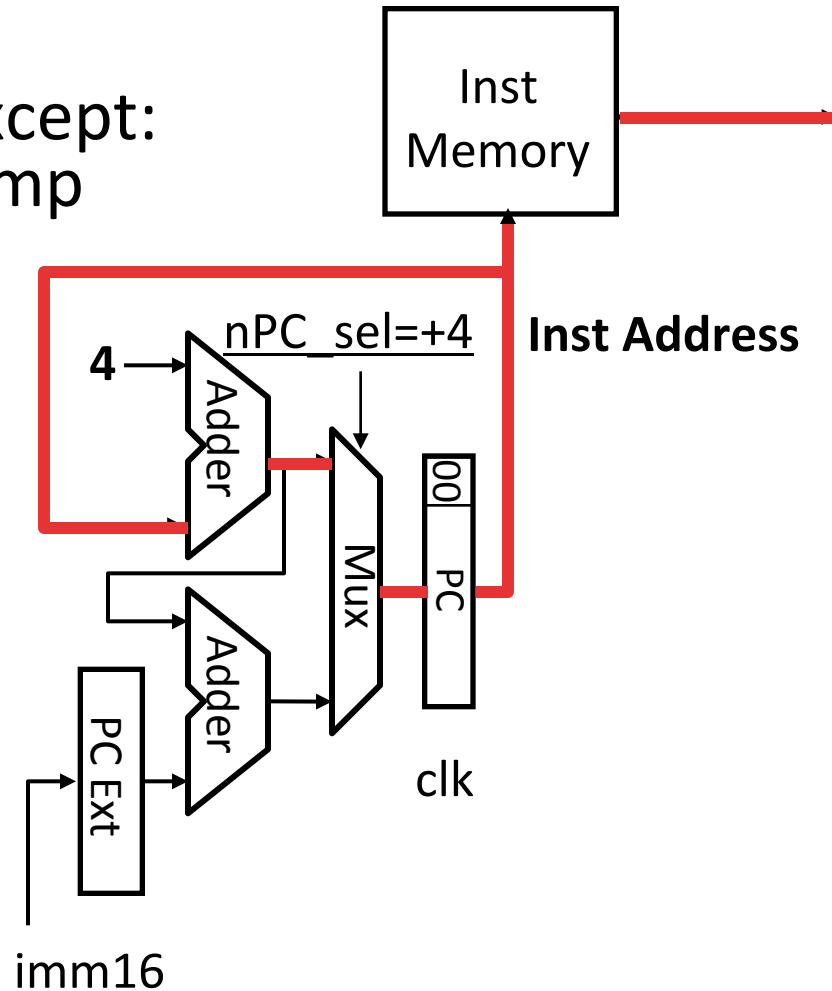
- $PC = PC + 4$
 - Same for all instructions except: Branch and Jump



Single Cycle Datapath during Jump



 
- New PC = { PC[31..28], target address, 00 }



Single Cycle Datapath during Jump



 
- New PC = { PC[31..28], target address, 00 }



Instruction Fetch Unit at the End of Jump



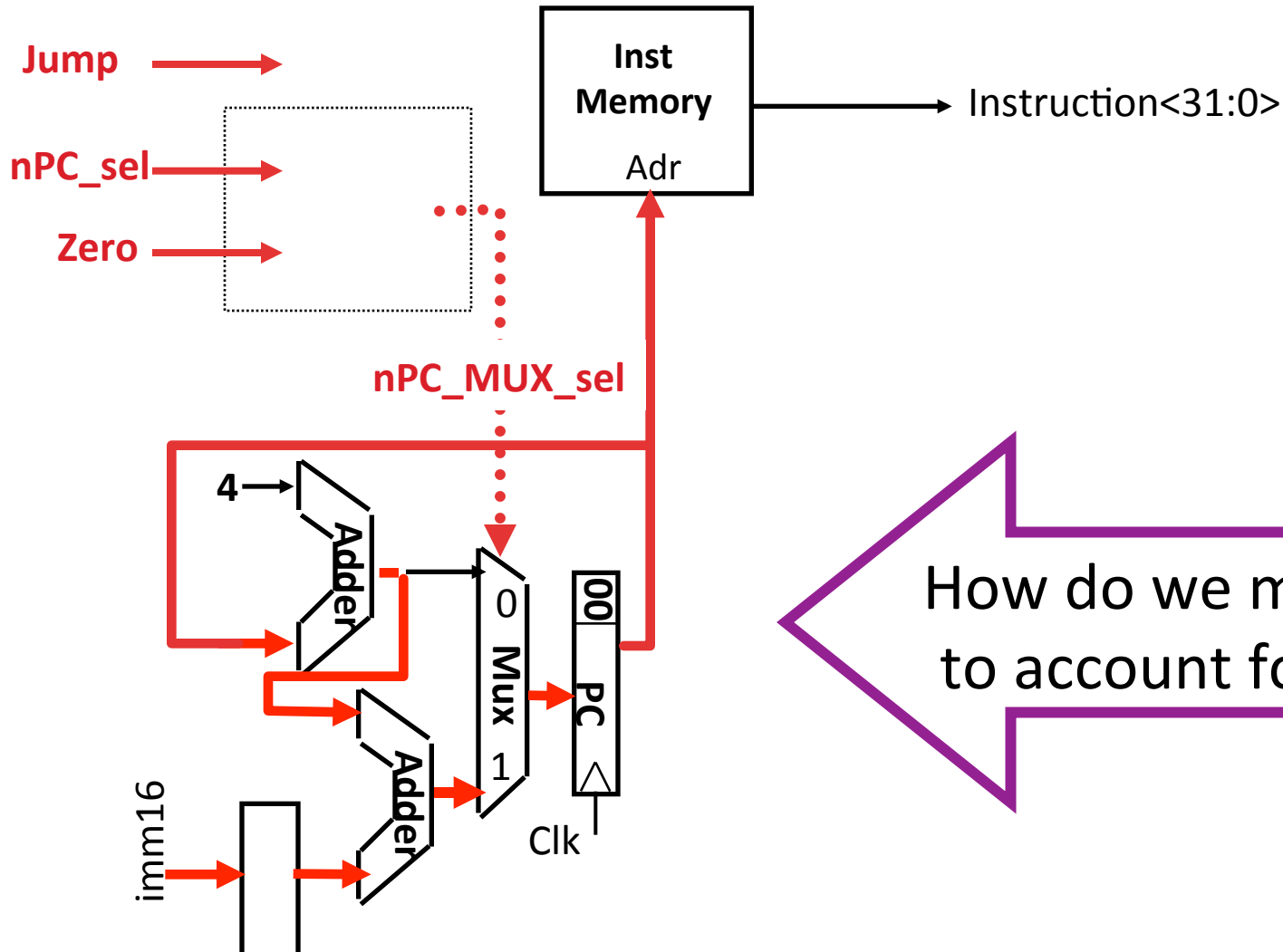- New PC = { PC[31..28], target address, 00 }




How do we modify this to account for jumps?

Instruction Fetch Unit at the End of Jump



 
- New PC = { PC[31..28], target address, 00 }



Clickers/Peer Instruction


What new instruction would need no new datapath hardware?

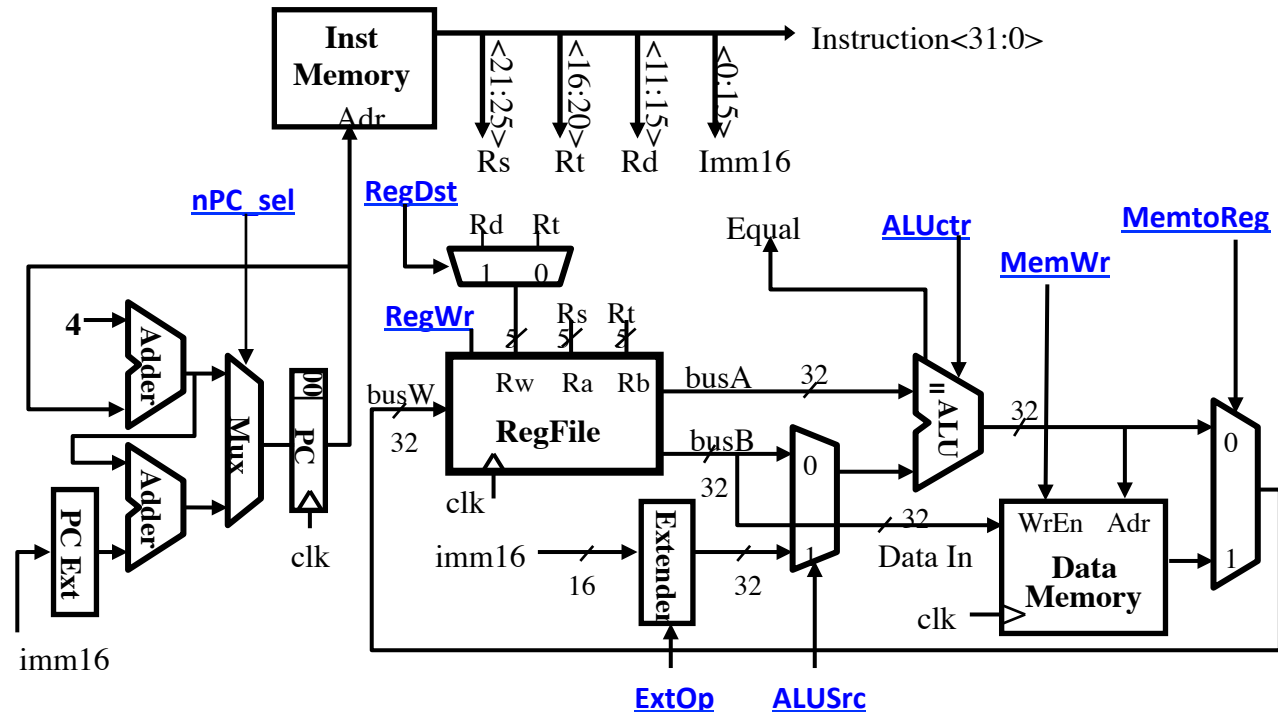- A: branch if reg==immediate
- B: add two registers and branch if result zero
- C: store with auto-increment of base address:
 - sw rt, rs, offset // rs incremented by offset after store
- D: shift left logical by one bit



In The News: Tile-Mx100

100 64-bit ARM cores on one chip

 


EZChip (bought Tiler)

100 64-bit ARM Cortex A53

- Dual-issue, in-order

Break

P&H Figure 4.17

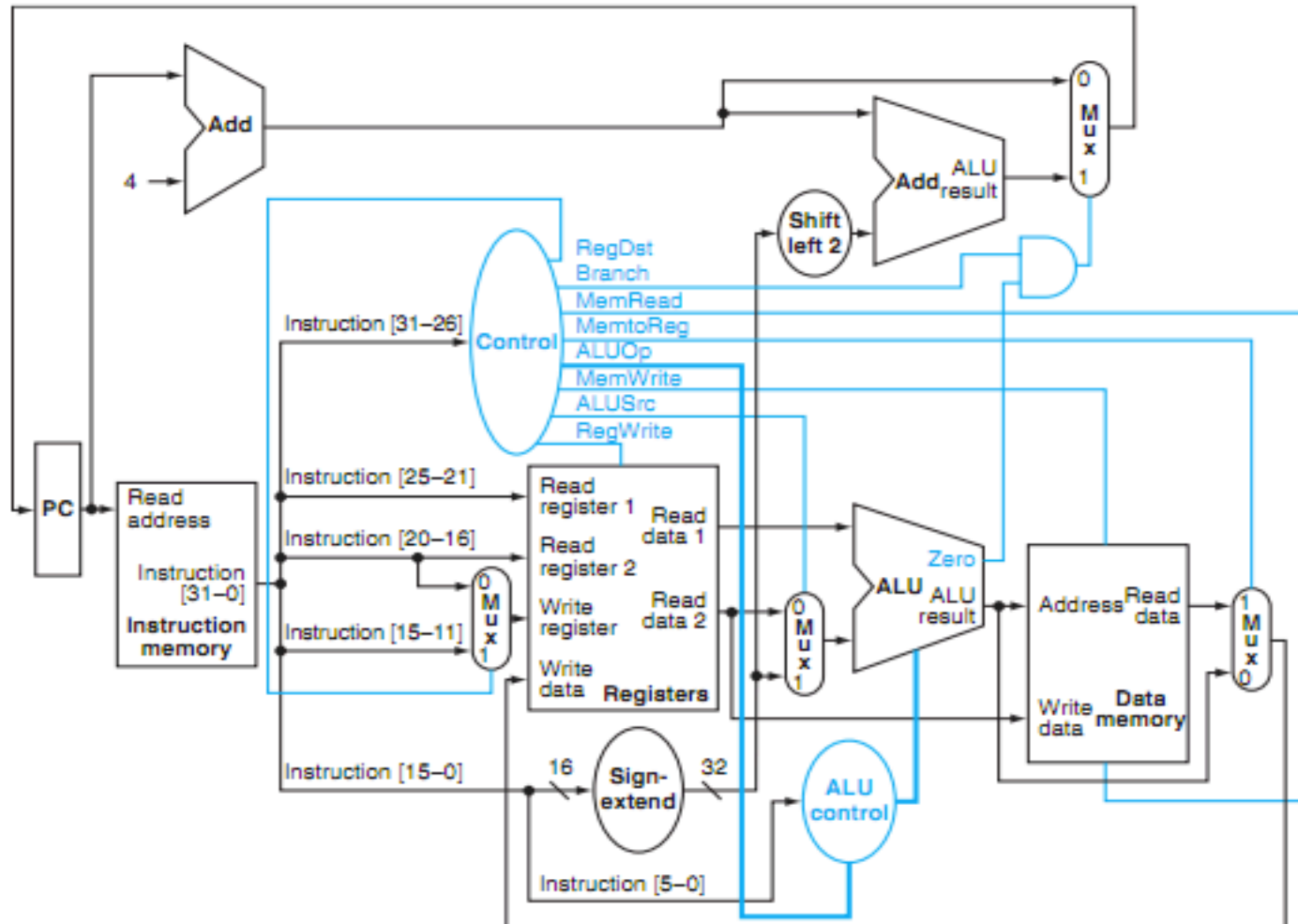

Summary of the Control Signals (1/2)

inst Register Transfer

add $R[rd] \leftarrow R[rs] + R[rt]; PC \leftarrow PC + 4$
 ALUSrc=RegB, ALUctr="ADD", RegDst=rd, RegWr, nPC_sel="+4"

sub $R[rd] \leftarrow R[rs] - R[rt]; PC \leftarrow PC + 4$
 ALUSrc=RegB, ALUctr="SUB", RegDst=rd, RegWr, nPC_sel="+4"

ori $R[rt] \leftarrow R[rs] + \text{zero_ext}(\text{Imm16}); PC \leftarrow PC + 4$
 ALUSrc=Im, Extop="Z", ALUctr="OR", RegDst=rt, RegWr, nPC_sel="+4"

lw $R[rt] \leftarrow \text{MEM}[R[rs] + \text{sign_ext}(\text{Imm16})]; PC \leftarrow PC + 4$
 ALUSrc=Im, Extop="sn", ALUctr="ADD", MemtoReg, RegDst=rt, RegWr,
 nPC_sel = "+4"

sw $\text{MEM}[R[rs] + \text{sign_ext}(\text{Imm16})] \leftarrow R[rs]; PC \leftarrow PC + 4$
 ALUSrc=Im, Extop="sn", ALUctr = "ADD", MemWr, nPC_sel = "+4"

beq if ($R[rs] == R[rt]$) then $PC \leftarrow PC + \text{sign_ext}(\text{Imm16})$ || 00
 else $PC \leftarrow PC + 4$
 nPC_sel = "br", ALUctr = "SUB"

Summary of the Control Signals (2/2)

See Appendix A

func

op

	10 0000	10 0010	We Don't Care :-)				
	00 0000	00 0000	00 1101	10 0011	10 1011	00 0100	00 0010
	add	sub	ori	lw	sw	beq	jump
RegDst	1	1	0	0	x	x	x
ALUSrc	0	0	1	1	1	0	x
MemtoReg	0	0	0	1	x	x	x
RegWrite	1	1	1	1	0	0	0
MemWrite	0	0	0	0	1	0	0
nPCsel	0	0	0	0	0	1	?
Jump	0	0	0	0	0	0	1
ExtOp	x	x	0	1	1	x	x
ALUctr<2:0>	Add	Subtract	Or	Add	Add	Subtract	x

	31	26	21	16	11	6	0						
R-type	op		rs		rt		rd		shamt		funct		add, sub
I-type	op		rs		rt		immediate						ori, lw, sw, beq
J-type	op		target address										jump

Boolean Expressions for Controller

```
RegDst      = add + sub
ALUSrc      = ori + lw + sw
MemtoReg    = lw
RegWrite    = add + sub + ori + lw
MemWrite    = sw
nPCsel      = beq
Jump        = jump
ExtOp       = lw + sw
ALUctr[0]   = sub + beq    (assume ALUctr is 00 ADD, 01 SUB, 10 OR)
ALUctr[1]   = or
```


Where:

```
rtype = ~op5 • ~op4 • ~op3 • ~op2 • ~op1 • ~op0,
ori    = ~op5 • ~op4 • op3 • op2 • ~op1 • op0
lw     = op5 • ~op4 • ~op3 • ~op2 • op1 • op0
sw     = op5 • ~op4 • op3 • ~op2 • op1 • op0
beq    = ~op5 • ~op4 • ~op3 • op2 • ~op1 • ~op0
jump   = ~op5 • ~op4 • ~op3 • ~op2 • op1 • ~op0
```

```
add = rtype • func5 • ~func4 • ~func3 • ~func2 • ~func1 • ~func0
sub = rtype • func5 • ~func4 • ~func3 • ~func2 • func1 • ~func0
```

How do we
implement this in
gates?

Controller Implementation

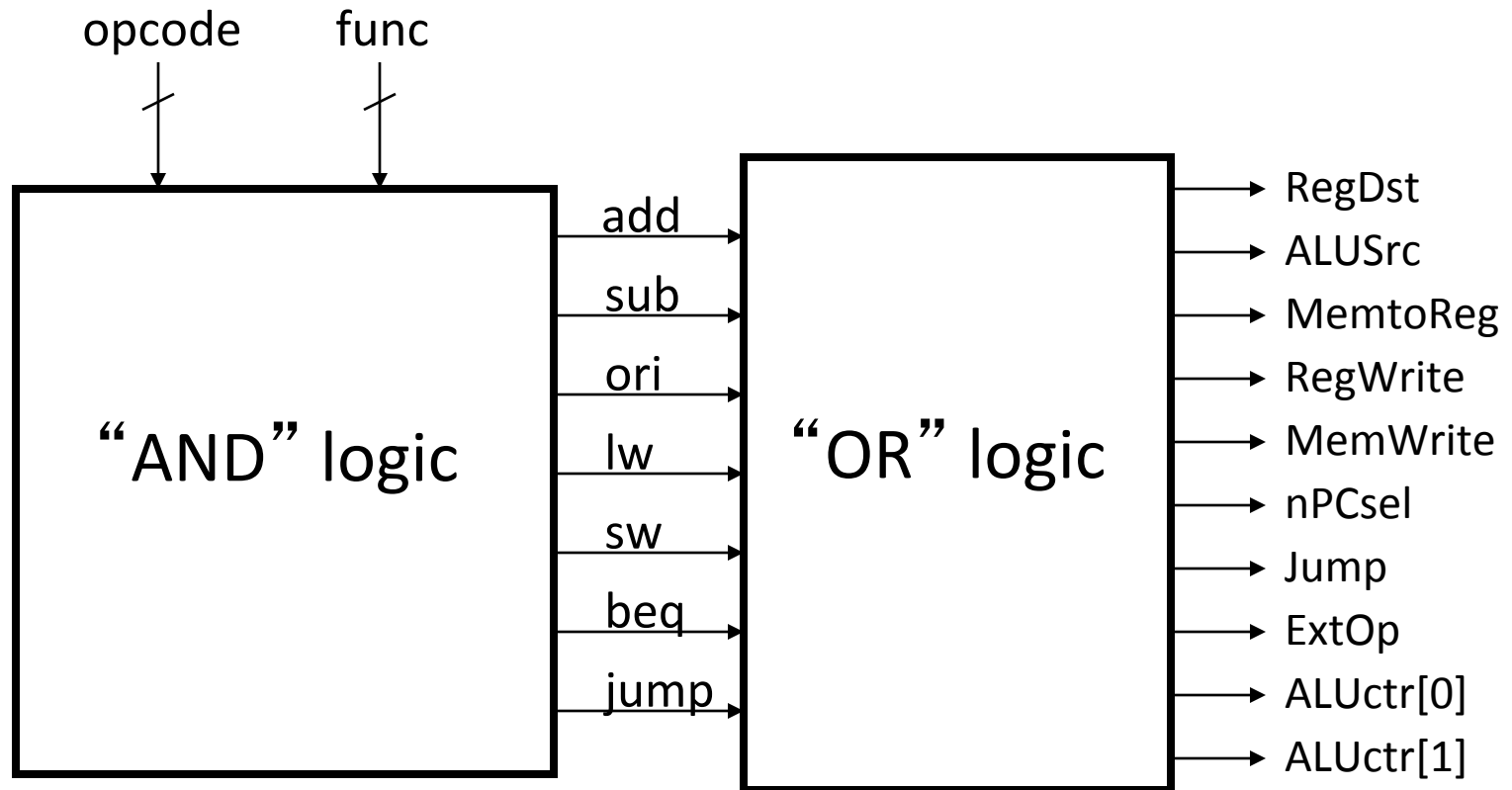

Clicker Question

Which of the following is TRUE?

- A. The CPU's control needs only opcode/funct to determine the next PC value to select
- B. The clock can have a shorter period for instructions that don't use memory
- C. The CPU requires a separate instruction memory and data memory
- D. The ALU is used to set PC to PC+4 when necessary

Summary: Single-cycle Processor

- Five steps to design a processor:

1. Analyze instruction set → datapath requirements
2. Select set of datapath components & establish clock methodology
3. Assemble datapath meeting the requirements
4. Analyze implementation of each instruction to determine setting of control points that effects the register transfer.
5. Assemble the control logic
 - Formulate Logic Equations
 - Design Circuits

